

# Spectrum Analyzer Range Extender

Scott Littfin


NOEDV



Galaxy A42 5G
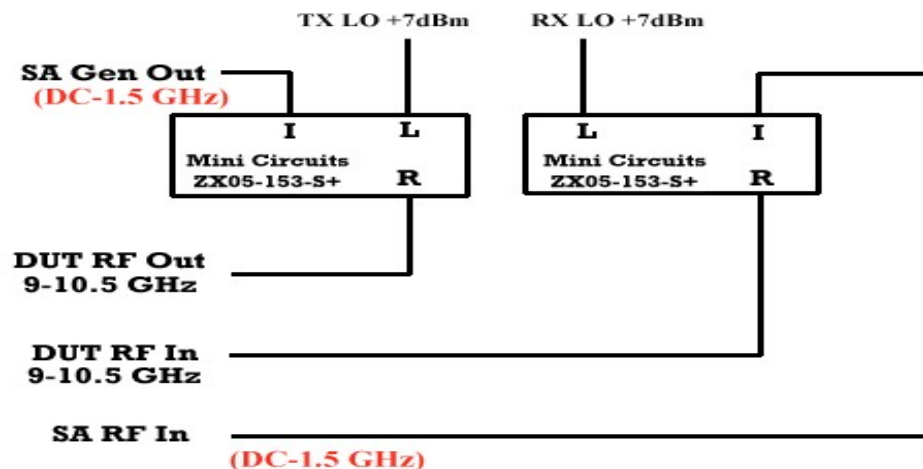
## Overview.

The spectrum analyzer range extender is used to extend the frequency range of the base spectrum analyzer. The unit accomplishes this by the use of mixers that up-convert the tracking generator output from the spectrum analyzer to desired frequency ranges and down-convert desired frequency ranges to the base frequency range of the spectrum analyzer.




### 9-10.5 GHz Converter Section


SA=Spectrum Analyzer

DUT=Device Under Test

LO=9000 MHz (for SA range 9.0-10.5 GHz)

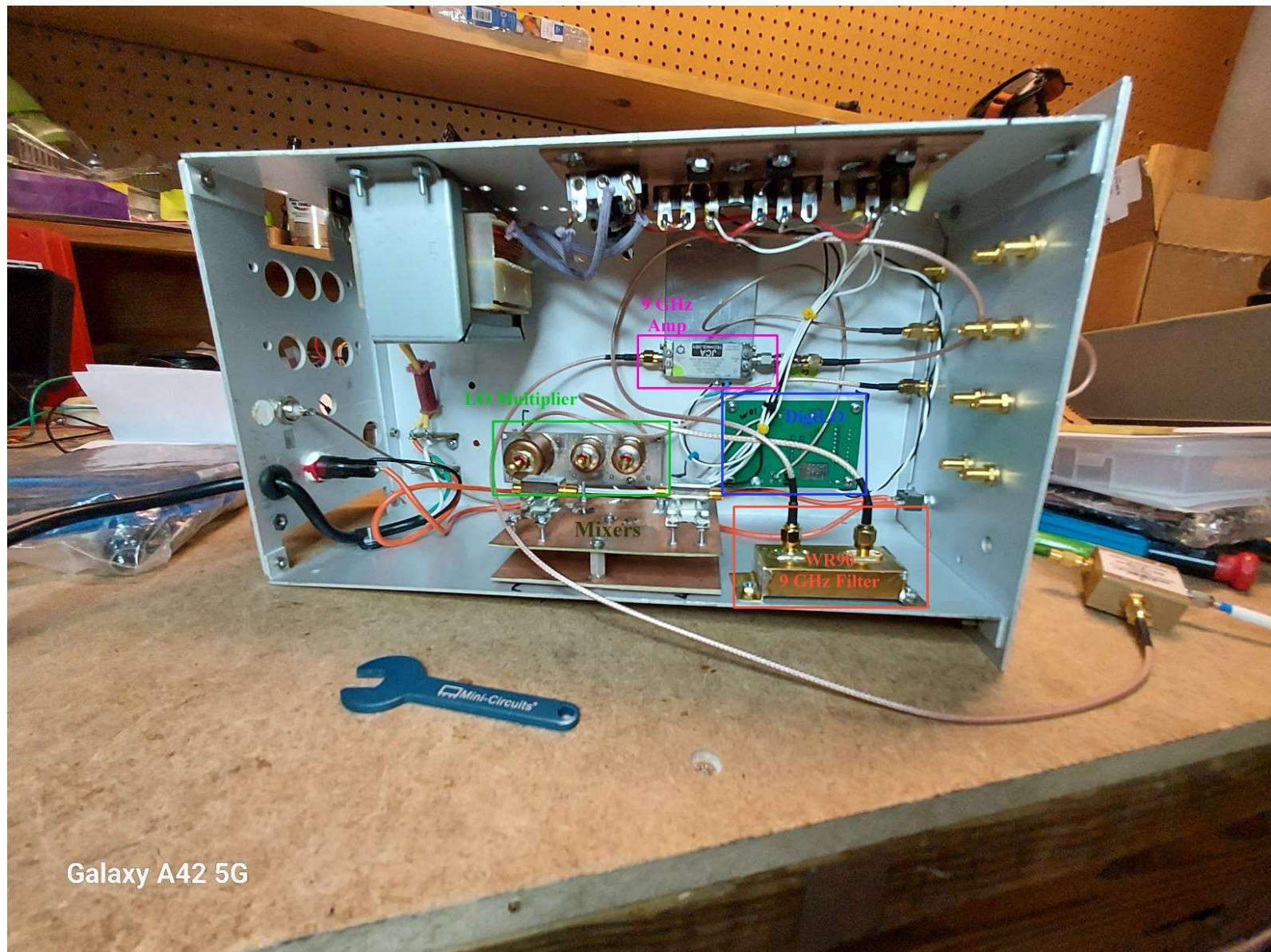

Galaxy A42 5G

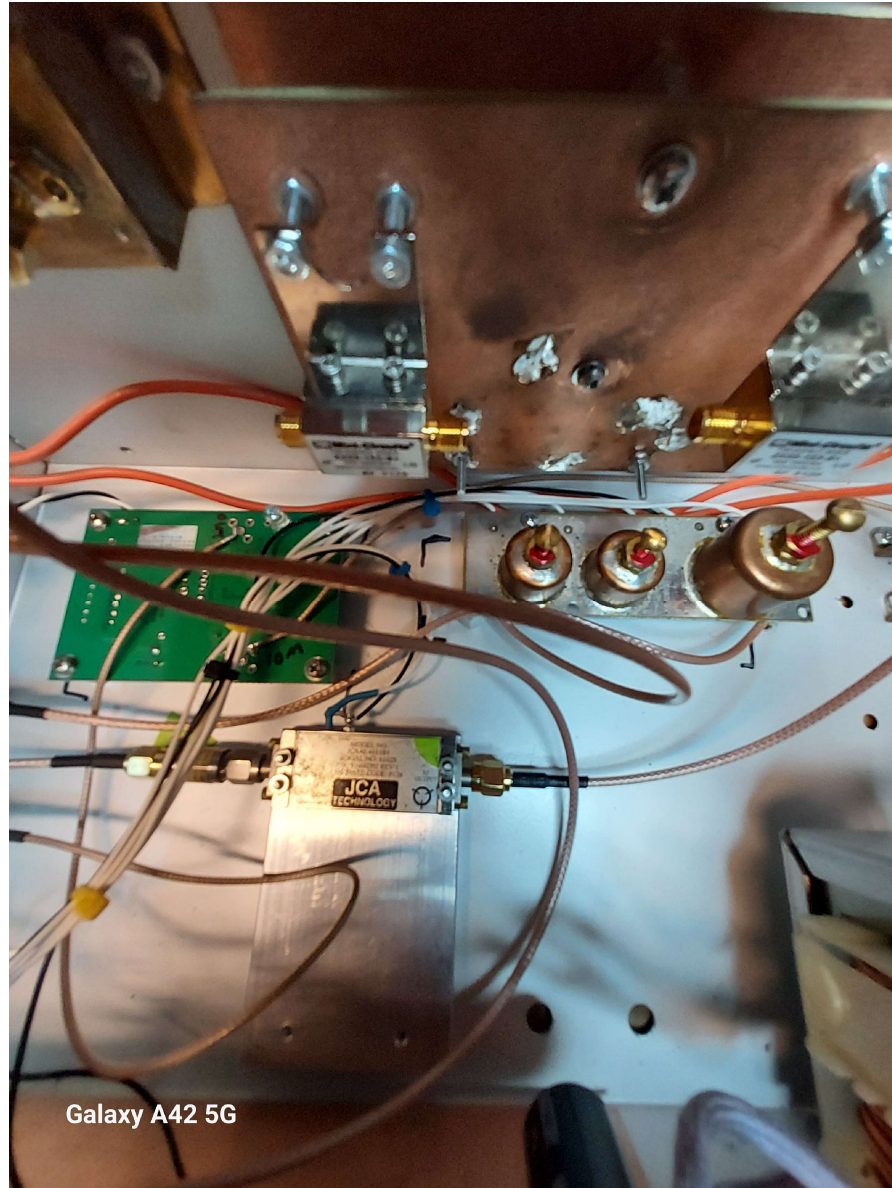

Galaxy A42 5G

# Theory of Operation (9-10.5 GHz)

- In principle, the unit is quite simple. It is basically a transverter system. It utilizes a DigiLO PLL synthesizer board to supply a signal at 1000 MHz (one of the standard frequencies programmed into it) at approximately the 0 dBm level. This signal drives a W1GHZ 10 GHz Personal Beacon Board, which triples it to 3000 MHz and finally triples it again to supply a 9000 MHz signal at +5 to +10 dBm. This is the perfect level to drive the mixers I used (Minicircuits ZX05-153-S+). My output from the W1GHz board was considerably less, so I ended up adding a small JCA amplifier from eBay to get it up to just under +10 dBm.




Galaxy A42 5G
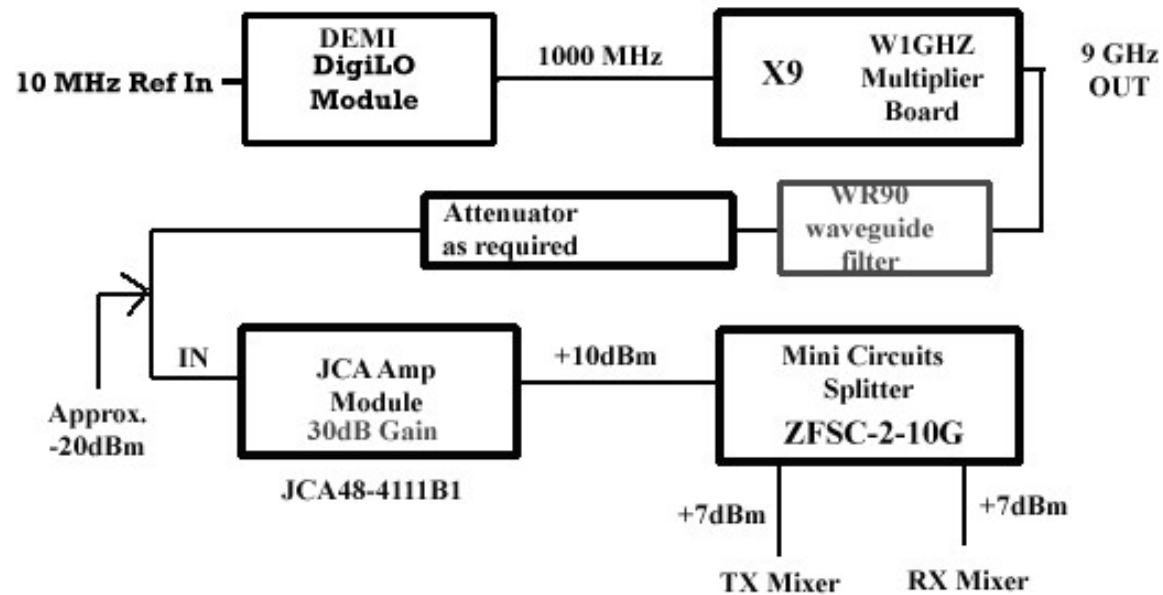
## The LO Section

The 9 GHz LO signal from the W1GHZ board is passed through a homebrew high pass filter made with a short section of WR90 waveguide with SMA connectors soldered at each end and the ends shorted with pieces of brass sheet. The signal out of the filter is connected to the JCA amp and then to the LO port of the mixers via a splitter. There are two mixers used. One up converts the Tracking Generator output of the spectrum analyzer up from its base range (0-1500 MHz) to 9-10.5 GHz. The other mixer down converts signals in the 9-10.5 GHz range to the base range of the spectrum analyzer.






## 9 GHz LO SECTION
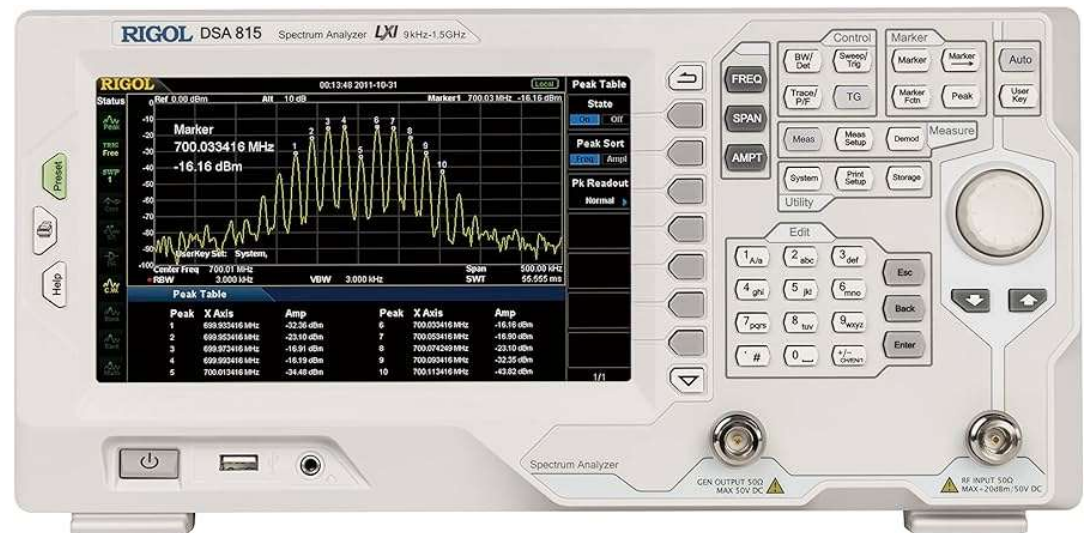
# Rigol Spectrum Analyzer

I have a Rigol DSA-815 with the tracking generator option. I bought it brand new from a seller on eBay for \$999. Cheap at half the price! Wait, is that right? No...cheap at TWICE the price! Anyway, it's a great starter spectrum analyzer that is easy to use and offers some nice features. One is that you can manually set a "Frequency Offset" which mathematically calculates the frequencies displayed to a more useful value. In this project, I set this offset to 9000 MHz (LO Frequency) so that I can enter or display frequencies directly.



Questions?

The End